

Lab 3 Report

ECE 124

Group 3 Session 201

Nandita Lohani

Puneet Bhullar

Magnitude Comparator Truth Table

Comparison Inputs from 1-Bit Comparators												4-Bit Comparator Outputs		
A3<B3	A3=B3	A3>B3	A2<B2	A2=B2	A2>B2	A1<B1	A1=B1	A1>B1	A0<B0	A0=B0	A0>B0	A<B	A=B	A>B
0	0	1	X	X	X	X	X	X	X	X	X	0	0	1
1	0	0	X	X	X	X	X	X	X	X	X	1	0	0
0	1	0	0	0	1	X	X	X	X	X	X	0	0	1
0	1	0	1	0	0	X	X	X	X	X	X	1	0	0
0	1	0	0	1	0	0	0	1	X	X	X	0	0	1
0	1	0	0	1	0	1	0	0	X	X	X	1	0	0
0	1	0	0	1	0	0	1	0	0	0	1	0	0	1
0	1	0	0	1	0	0	1	0	1	0	0	1	0	0
0	1	0	0	1	0	0	1	0	0	1	0	0	1	0


Single Bit Magnitude Comparator (CompX1)

```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar
2  library ieee;
3  use ieee.std_logic_1164.all;
4  use ieee.numeric_std.all;
5
6  -----
7  entity CompX1 is
8  port (
9      A, B : in std_logic;
10     AgreatB, AequalB, AlesB : out std_logic
11 );
12 end CompX1;
13
14 -- *****
15 -- * Architecture *
16 -- *****
17
18 architecture Single_Bit_Comparator of CompX1 is
19
20 begin
21
22     -- boolean logic applied to each output with input operands
23
24     AgreatB <= A and (not B);
25     AequalB <= A xnor B;
26     AlesB <= (not A) and B;
27
28 end architecture Single_Bit_Comparator;
29
30 -----
```

4-Bit Magnitude Comparator (Comp4)


```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar
2  library ieee;
3  use ieee.std_logic_1164.all;
4  use ieee.numeric_std.all;
5  -----
6  entity Comp4 is
7  port (
8      A, B : in std_logic_vector(3 downto 0);
9      AGTB_out, AEQB_out, ALTB_out : out std_logic
10 );
11 end Comp4;
12
13 -- *****
14 architecture Four_Bit_Comparator of Comp4 is
15 component Comp1
16 port (
17     A, B : in std_logic;
18     AgreatB, AequalB, AlesB : out std_logic
19 );
20 end component;
21
22
23
24 signal AGTB, AEQB, ALTB : std_logic_vector (3 downto 0);
25 begin
26
27     -- Outputs expressed as boolean equations of operand inputs
28
29     AGTB_out <= ((AGTB(3)) or
30                 (AEQB(3) and AGTB(2)) or
31                 (AEQB(3) and AEQB(2) and AGTB(1)) or
32                 (AEQB(3) and AEQB(2) and AEQB(1) and AGTB(0))
33 );
34
35     AEQB_out <= (AEQB(3) and AEQB(2) and AEQB(1) and AEQB(0));
36
37
38     ALTB_out <= ((ALTB(3)) or
39                 (AEQB(3) and ALTB(2)) or
40                 (AEQB(3) and AEQB(2) and ALTB(1)) or
41                 (AEQB(3) and AEQB(2) and AEQB(1) and ALTB(0))
42 );
43
44     -----instantiation of four single bit comparators-----
45
46     inst1: Comp1 port map (A(3), B(3), AGTB(3), AEQB(3), ALTB(3));
47     inst2: Comp1 port map (A(2), B(2), AGTB(2), AEQB(2), ALTB(2));
48     inst3: Comp1 port map (A(1), B(1), AGTB(1), AEQB(1), ALTB(1));
49     inst4: Comp1 port map (A(0), B(0), AGTB(0), AEQB(0), ALTB(0));
50
51 end architecture Four_Bit_Comparator;
52
53 -----
```

4-Bit Magnitude Comparator Simulation 1

 


Each output is activated at some point during the simulation with correct functionality.

4-Bit Magnitude Comparator Simulation 2

 


Each output is activated at some point during the simulation with correct functionality.

4-Bit Magnitude Comparator Simulation 3

 

Each output is activated at some point during the simulation with correct functionality.

4-Bit Magnitude Comparator Simulation 4

 

Each output is activated at some point during the simulation with correct functionality.

MUX File


```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar
2  library ieee;
3  use ieee.std_logic_1164.all;
4  library work;
5  -----
6  entity MUX is
7  port (
8      desired_temp, vacation_temp      : in std_logic_vector(3 downto 0);
9      vacation_mode                     : in std_logic;
10     mux_temp                          : out std_logic_vector(3 downto 0)
11 );
12
13 end entity MUX;
14 -----
15
16 architecture mux_logic of MUX is
17
18 begin
19
20     --for the multiplexing of two mux input busses
21     with vacation_mode select
22     mux_temp <= desired_temp when '0',
23                vacation_temp when '1';
24
25 end architecture mux_logic;
26
27
```

SevenSegment File

```

1  --Author: Group 3, Nandita Lohani, Puneet Bhullar
2  library ieee;
3  use ieee.std_logic_1164.all;
4  use ieee.numeric_std.all;
5
6  -----
7
8  entity SevenSegment is port (
9
10     hex      : in  std_logic_vector(3 downto 0);  -- The 4 bit data to be displayed
11
12     sevensseg : out std_logic_vector(6 downto 0)  -- 7-bit outputs to a 7-segment
13 );
14 end SevenSegment;
15
16 architecture decode_function1 of SevenSegment is
17
18     --
19     -- The following statements convert a 4-bit input, called dataIn to a pattern of 7 bits.
20     -- The segment turns on when it is '1' otherwise '0'.
21     --
22     begin
23         with hex select
24             sevensseg(6 downto 0);
25
26         --GFEDCBA      3210      -- data in
27         <="0111111" when "0000", -- [0]
28         "0000110" when "0001", -- [1]
29         "1011011" when "0010", -- [2]
30         "1001111" when "0011", -- [3]
31         "1100110" when "0100", -- [4]
32         "1101101" when "0101", -- [5]
33         "1111101" when "0110", -- [6]
34         "0000111" when "0111", -- [7]
35         "1111111" when "1000", -- [8]
36         "1101111" when "1001", -- [9]
37         "1110111" when "1010", -- [A]
38         "1111100" when "1011", -- [b]
39         "1011000" when "1100", -- [c]
40         "1011110" when "1101", -- [d]
41         "1111001" when "1110", -- [E]
42         "1110001" when "1111", -- [F]
43         "0000000" when others;  -- [ ]
44
45     end architecture decode_function1;
46
47     -----

```

 

Segment7_mux File

```
38  --Author: Group 3, Nandita Lohani, Puneet Bhullar
39  library IEEE;
40  use IEEE.std_logic_1164.all;
41  use IEEE.numeric_std.all;
42
43  -- Entity
44  -- *****
45  [
46  entity segment7_mux is
47  port (
48      clk      : in  std_logic := '0';
49      DIN2     : in  std_logic_vector(6 downto 0);
50      DIN1     : in  std_logic_vector(6 downto 0);
51      DOUT     : out std_logic_vector(6 downto 0);
52      DIG2     : out std_logic;
53      DIG1     : out std_logic;
54  );
55  end entity segment7_mux;
56  -- *****
57
58  architecture syn of segment7_mux is
59
60      signal toggle      : std_logic;
61      signal DOUT_TEMP   : std_logic_vector(6 downto 0);
62
63  begin
64      [
65      -- Register File
66      ]
67      clk_proc:process(CLK)
68      variable COUNT      : unsigned(10 downto 0) := "00000000000";
69      begin
70          if (rising_edge(CLK)) then
71              COUNT := COUNT + 1;
72          else
73              COUNT := COUNT;
74          end if;
75          toggle <= COUNT(10);
76          end process clk_proc;
77          DIG1 <= NOT toggle;
78          DIG2 <= toggle;
79
80          DOUT_TEMP(0) <= (DIN2(0)) WHEN (toggle = '1') ELSE (DIN1(0));
81          DOUT_TEMP(1) <= (DIN2(1)) WHEN (toggle = '1') ELSE (DIN1(1));
82          DOUT_TEMP(2) <= (DIN2(2)) WHEN (toggle = '1') ELSE (DIN1(2));
83          DOUT_TEMP(3) <= (DIN2(3)) WHEN (toggle = '1') ELSE (DIN1(3));
84          DOUT_TEMP(4) <= (DIN2(4)) WHEN (toggle = '1') ELSE (DIN1(4));
85          DOUT_TEMP(5) <= (DIN2(5)) WHEN (toggle = '1') ELSE (DIN1(5));
86          DOUT_TEMP(6) <= (DIN2(6)) WHEN (toggle = '1') ELSE (DIN1(6));
87          -- DOUT_TEMP(7) <= (DIN2(7)) WHEN (toggle = '1') ELSE (DIN1(7));
88      ]
89  end architecture;
```

Segment7_mux File Cont.

```
89     DOUT(0) <= '0' WHEN (DOUT_TEMP(0) = '0') ELSE '1';
90     DOUT(1) <= '0' WHEN (DOUT_TEMP(1) = '0') ELSE 'Z'; --open drain
91     DOUT(2) <= '0' WHEN (DOUT_TEMP(2) = '0') ELSE '1';
92     DOUT(3) <= '0' WHEN (DOUT_TEMP(3) = '0') ELSE '1';
93     DOUT(4) <= '0' WHEN (DOUT_TEMP(4) = '0') ELSE '1';
94     DOUT(5) <= '0' WHEN (DOUT_TEMP(5) = '0') ELSE 'Z'; --open drain
95     DOUT(6) <= '0' WHEN (DOUT_TEMP(6) = '0') ELSE 'Z'; --open drain
96     -- DOUT(7) <= '0' WHEN (DOUT_TEMP(7) = '0') ELSE '1';
97
98 end architecture syn;
```

Inverter File

```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar
2  library ieee;
3  use ieee.std_logic_1164.all;
4  library work;
5  -----
6  entity Inverter is
7  port (
8      pb_n0, pb_n1, pb_n2, pb_n3          : in std_logic;
9      pb_n0out, pb_n1out, pb_n2out, pb_n3out : out std_logic
10 );
11
12 end entity Inverter;
13 -----
14 architecture inverter_logic of Inverter is
15 begin
16     --- Ouputs with correct boolean equations using input operands
17
18     pb_n0out <= not pb_n0;
19     pb_n1out <= not pb_n1;
20     pb_n2out <= not pb_n2;
21     pb_n3out <= not pb_n3;
22
23 end architecture inverter_logic;
```

HVAC File

```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar
2  library ieee;
3  use ieee.std_logic_1164.all;
4  use ieee.numeric_std.all;
5  --*****
6  -- clk input is the LogicalStep 50MHz clock input
7  entity HVAC is
8  |
9  |   port
10 |   (
11 |       HVAC_SIM          : in boolean;
12 |       clk                : in std_logic;
13 |       run_n              : in std_logic;
14 |       increase, decrease : in std_logic;
15 |       temp               : out std_logic_vector (3 downto 0)
16 |   );
17 |
18 | end entity;
19 | --*****
20 | architecture rtl of HVAC is
21 | |
22 | |   signal clk_2hz          : std_logic;
23 | |   signal HVAC_clock       : std_logic;
24 | |   signal digital_counter : std_logic_vector(23 downto 0);
25 | |
26 | |   --*****
27 | |   begin
28 | |       -- clk_divider process generates a 2Hz Clk from the 50 Mhz clk
29 | |
30 | |   clk_divider: process (clk)
31 | |       variable counter : unsigned(23 downto 0);
32 | |
33 | |       begin
34 | |           -- Synchronously update counter
35 | |           if (rising_edge(clk)) then
36 | |               counter := counter + 1;
37 | |           end if;
38 | |           digital_counter <= std_logic_vector(counter);
39 | |       end process;
40 | |
41 | |   end architecture;
42 |
```

HVAC File Cont.

```
42 |
43 | clk_2hz <= digital_counter(23);
44 |
45 | clk_mux: process (HVAC_SIM)
46 | | begin
47 | | | if (HVAC_SIM) then
48 | | | | HVAC_clock <= clk;
49 | | | | else
50 | | | | | HVAC_clock <= clk_2hz;
51 | | | | end if;
52 | | end process;
53 |
54 |
55 | counter: process (HVAC_clock)
56 | | variable cnt : unsigned(3 downto 0) := "0111";
57 | | begin
58 | |
59 | | -- Synchronously update counter
60 | | | if ((rising_edge(HVAC_clock)) AND (run_n = '0')) then
61 | | | |
62 | | | | | if ((increase = '1') AND (cnt /= 15)) then
63 | | | | | | -- Increment only if not at maxvalue
64 | | | | | | cnt := cnt + 1;
65 | | | | | elsif ((decrease = '1') AND (cnt /= 0)) then
66 | | | | | | -- Decrement only if not at minvalue
67 | | | | | | cnt := cnt - 1;
68 | | | | | end if;
69 | | | |
70 | | | | end if;
71 | | |
72 | | | -- Output the current count
73 | | | temp <= std_logic_vector(cnt);
74 | | end process;
75 |
76 | end rtl;
```

TESTER File

```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar
2  library ieee;
3  use ieee.std_logic_1164.all;
4  -----
5
6  entity Tester is port (
7      MC_TESTMODE      : in  std_logic;
8      I1EQI2,I1GTI2,I1LTI2 : in  std_logic;
9      input1            : in  std_logic_vector(3 downto 0);
10     input2            : in  std_logic_vector(3 downto 0);
11     TEST_PASS         : out std_logic
12 );
13 end Tester;
14 -----
15
16 architecture Test_ckt of Tester is
17
18     signal EQ_PASS, GT_PASS, LT_PASS : std_logic;
19
20 begin
21     Tester1:
22     process (MC_TESTMODE, input1, input2, I1EQI2, I1GTI2, I1LTI2) is
23     begin
24
25         IF ((input1 = input2) AND (I1EQI2 = '1')) THEN
26             EQ_PASS <= '1';
27             GT_PASS <= '0';
28             LT_PASS <= '0';
29         ELSEIF ((input1 > input2) AND (I1GTI2 = '1')) THEN
30             GT_PASS <= '1';
31             EQ_PASS <= '0';
32             LT_PASS <= '0';
33         ELSEIF ((input1 < input2) AND (I1LTI2 = '1')) THEN
34             LT_PASS <= '1';
35             EQ_PASS <= '0';
36             GT_PASS <= '0';
37         ELSE
38             EQ_PASS <= '0';
39             GT_PASS <= '0';
40             LT_PASS <= '0';
41         END IF;
42         TEST_PASS <= MC_TESTMODE AND (EQ_PASS OR GT_PASS OR LT_PASS);
43     end process;
44 end;
```


Energy Monitor Control File

```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar
2  library ieee;
3  use ieee.std_logic_1164.all;
4  use ieee.numeric_std.all;
5
6  -----
7  entity Energy_Monitor is
8  port (
9      AGTB, AEQB, ALTB, vacation_mode, MC_test, window_open, door_open : in std_logic;
10     furnace, at_temp, AC, blower, window, door, vacation: out std_logic;
11     run_n, increase, decrease : out std_logic
12 );
13 end Energy_Monitor;
14
15 -- *****
16 -- * Architecture
17 -- *****
18
19 architecture Energy_Monitoring_Controller of Energy_Monitor is
20     signal activate: std_logic;
21
22     -----
23
24 begin
25     energymonitor1:
26
27     process (AGTB, AEQB, ALTB, vacation_mode, MC_test, window_open, door_open) is
28     begin
29         --- Outputs expressed as correct boolean expressions with input operands and signals
30
31         furnace <= ((AGTB) and (not MC_test) and (not window_open) and (not door_open));
32         at_temp <= AEQB;
33         AC <= ((ALTB) and (not MC_test) and (not window_open) and (not door_open));
34         blower <= ((AGTB or ALTB) and (not MC_test) and (not window_open) and (not door_open));
35         window <= window_open;
36         door <= door_open;
37         vacation <= vacation_mode;
38
39         decrease <= ALTB;
40         increase <= AGTB;
41         run_n <= ((AEQB) or (window_open) or (door_open) or (MC_test));
42
43     end process;
44
45 end architecture Energy_Monitoring_Controller;
46
47 -----
48
```

Logical Step Top

```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar
2  library ieee;
3  use ieee.std_logic_1164.all;
4  -----
5  entity LogicalStep_Lab3_top is port (
6      clk_in_50      : in  std_logic;
7      pb_n           : in  std_logic_vector(3 downto 0);
8      sw             : in  std_logic_vector(7 downto 0);
9  )
10 -----
11      --HVAC_temp : out std_logic_vector(3 downto 0); -- used for simulations only. Comment out for FPGA download compiles.
12 -----
13      leds        : out std_logic_vector(7 downto 0);
14      seg7_data   : out std_logic_vector(6 downto 0); -- 7-bit outputs to a 7-segment
15      seg7_char1  : out std_logic;                  -- seg7 digit1 selector
16      seg7_char2  : out std_logic;                  -- seg7 digit2 selector
17  );
18  end LogicalStep_Lab3_top;
19
20 architecture design of LogicalStep_Lab3_top is
21
22     --
23     -- Provided Project Components Used
24     -----
25     component SevenSegment port (
26         hex      : in  std_logic_vector(3 downto 0); -- The 4 bit data to be displayed
27         sevenseg : out std_logic_vector(6 downto 0); -- 7-bit outputs to a 7-segment
28     );
29     end component SevenSegment;
30
31     component segment7_mux port (
32         clk      : in  std_logic := '0';
33         DIN2     : in  std_logic_vector(6 downto 0);
34         DIN1     : in  std_logic_vector(6 downto 0);
35         DOUT     : out std_logic_vector(6 downto 0);
36         DIG2     : out std_logic;
37         DIG1     : out std_logic;
38     );
39     end component segment7_mux;
40     -----
41     component Tester port (
42         MC_TESTMODE : in  std_logic;
43         I1EQI2,I1GTI2,I1LTI2 : in  std_logic;
44         input1      : in  std_logic_vector(3 downto 0);
45         input2      : in  std_logic_vector(3 downto 0);
46         TEST_PASS   : out std_logic;
47     );
48     end component;
49
```


Logical Step Top Cont.

```
50 -----
51 component HVAC port (
52     HVAC_SIM      : in boolean;
53     clk            : in std_logic;
54     run_n          : in std_logic;
55     increase, decrease : in std_logic;
56     temp           : out std_logic_vector (3 downto 0)
57 );
58 end component;
59 -----
60 component Comp4 port (
61     A, B : in std_logic_vector(3 downto 0);
62     AGTB_out, AEQB_out, ALTB_out : out std_logic
63 );
64 end component;
65 -----
66 component MUX port (
67     vacation_mode      : in std_logic;
68     desired_temp, vacation_temp : in std_logic_vector(3 downto 0);
69     mux_temp           : out std_logic_vector(3 downto 0)
70 );
71 end component;
72 -----
73 component Inverter port (
74     pb_n0, pb_n1, pb_n2, pb_n3      : in std_logic;
75     pb_n0out, pb_n1out, pb_n2out, pb_n3out : out std_logic
76 );
77 end component;
78 -----
79 component Energy_Monitor port (
80     AGTB, AEQB, ALTB, vacation_mode, MC_test, window_open, door_open : in std_logic;
81     furnace, at_temp, AC, blower, window, door, vacation : out std_logic;
82     run_n, increase, decrease : out std_logic
83 );
84 end component;
85 -----
86 constant HVAC_SIM : boolean := FALSE; -- set to FALSE when compiling for FPGA download to LogicalStep board
87
88
89
90
```

Logical Step Top Cont.

```
91
92 -- global clock
93 signal clk_in : std_logic;
94 signal mux_temp, current_temp : std_logic_vector(3 downto 0);
95 signal mt_7seg, ct_7seg : std_logic_vector(6 downto 0);
96
97
98 --additional signals-----
99 signal desired_temp : std_logic_vector (3 downto 0);
100 signal vacation_temp : std_logic_vector (3 downto 0);
101 signal vacation_mode, MC_test_mode_signal, window_open, door_open : std_logic;
102 signal AGTB_signal, AEQB_signal, ALTB_signal : std_logic;
103 signal MC_test_pass : std_logic;
104 signal decrease, increase, run_n : std_logic;
105
106 -----
107 begin -- Here the circuit begins
108 clk_in <= clk_in_50; --hook up the clock input
109
110 -- temp inputs hook-up to internal busses.
111 desired_temp <= sw(3 downto 0);
112 vacation_temp <= sw(7 downto 4);
113
114 -----
115 --instantiation of all components with the appropriate singls and outputs
116 -----
117 inst1: sevensegment port map (mux_temp, mt_7seg);
118 inst2: sevensegment port map (current_temp, ct_7seg);
119
120 inst3: segment7_mux port map (clk_in, mt_7seg, ct_7seg, seg7_data, seg7_char2, seg7_char1);
121 inst4: Tester port map(MC_test_mode_signal, AEQB_signal, AGTB_signal, ALTB_signal, desired_temp, current_temp, leds(6));
122
123
124 inst5: HVAC port map (HVAC_SIM, clk_in, run_n, increase, decrease, current_temp );
125 inst6: Comp4 port map (mux_temp, current_temp, AGTB_signal, AEQB_signal, ALTB_signal);
126
127 inst7: MUX port map (vacation_mode, desired_temp, vacation_temp, mux_temp);
128
129 inst8: Inverter port map(pb_n(0), pb_n(1), pb_n(2), pb_n(3), door_open, window_open, MC_test_mode_signal, vacation_mode);
130
131 inst9: Energy_Monitor port map (AGTB_signal, AEQB_signal, ALTB_signal, vacation_mode, MC_test_mode_signal, window_open, door_open,
132                                leds(0), leds(1), leds(2), leds(3), leds(4), leds(5), leds(7), run_n, increase, decrease);
133
134 -----
135 --HVAC_temp <= current_temp; -- used for simulations only. Comment out for FPGA download compiles.
136
137 end design;
```


Energy Monitor Function Simulation 1

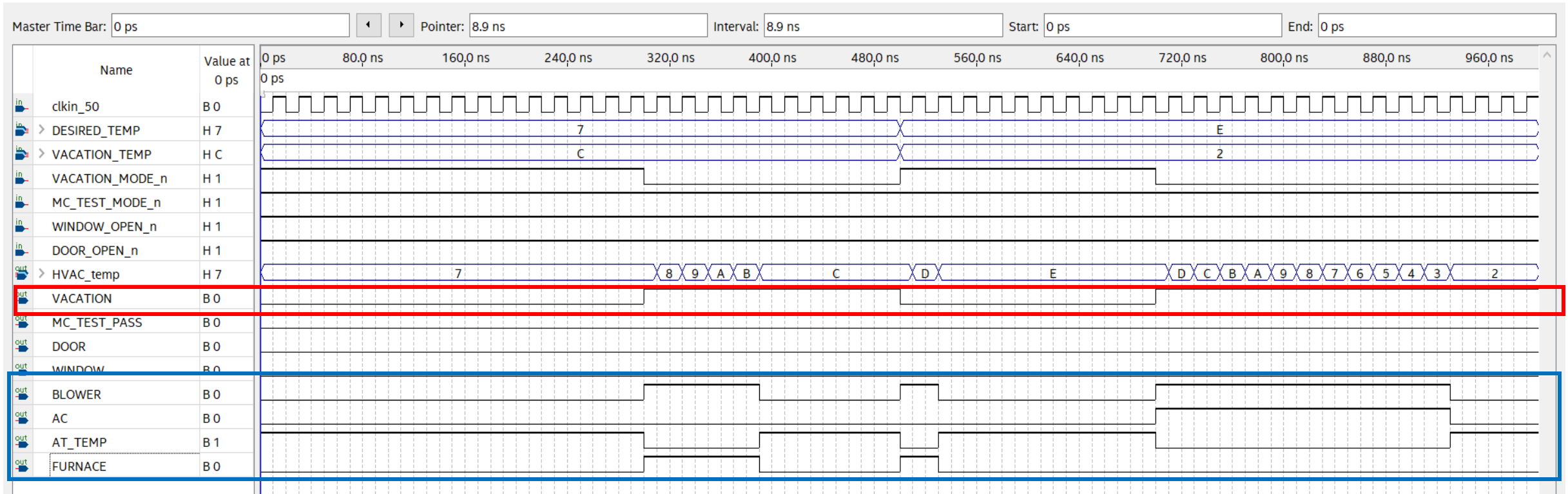


HVAC_temp changes to match the mux temp during vacation AND normal mode

furnace, AC, at_temp, blower function correctly in accordance with mux temp and current temp

Energy Monitor Function Simulation 2

 

Energy Monitor Function Simulation 3

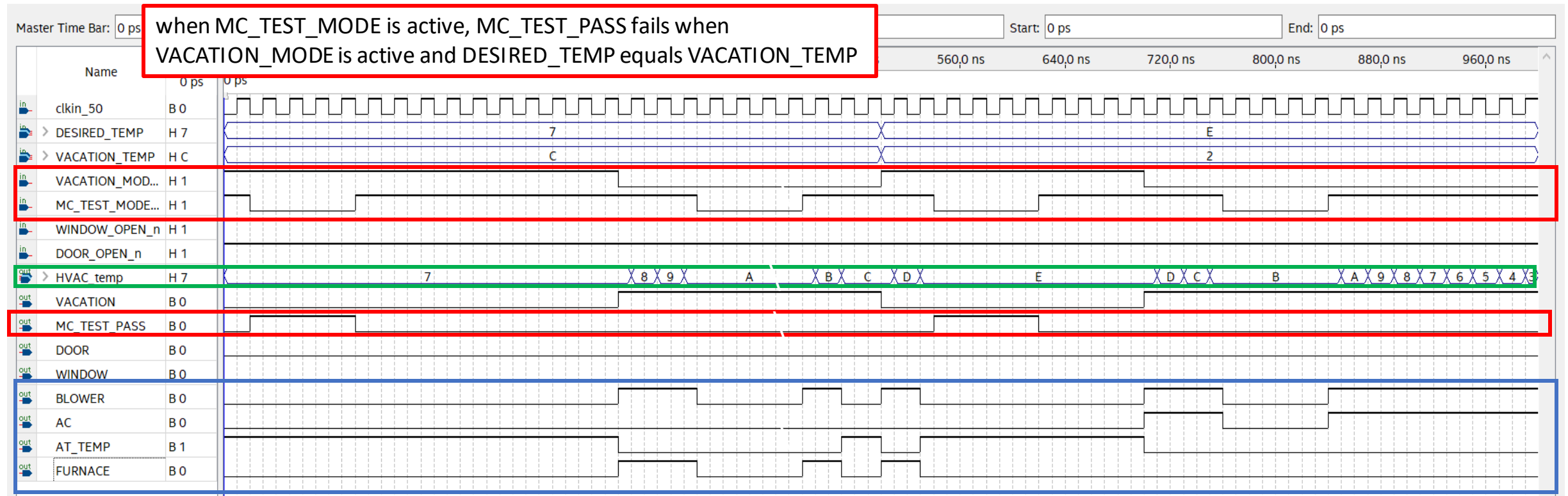

when MC_TEST_MODE is active, one of AC, AT_TEMP, FURNACE goes on during normal mode AND BLOWER is off

HVAC_TEMP stops changing when MC_TEST_MODE is active