

Lab 2 Report

ECE 124

Group 3 Session 201


Nandita Lohani

Puneet Bhullar

Hex Multiplexer File

```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar
2  library ieee;
3  use ieee.std_logic_1164.all;
4  library work;
5
6  entity hex_mux is
7  port (
8      hex_num3, hex_num2, hex_num1, hex_num0 : in std_logic_vector(3 downto 0);
9      mux_select                               : in std_logic_vector(1 downto 0);
10     hex_out                                  : out std_logic_vector(3 downto 0)
11 );
12
13 end entity hex_mux;
14
15 architecture mux_logic of hex_mux is
16 |
17 |
18 | begin
19 |
20 |     --for the multiplexing of four hex input busses
21 |     with mux_select(1 downto 0) select
22 |     hex_out <= hex_num0 when "00",
23 |                hex_num1 when "01",
24 |                hex_num2 when "10",
25 |                hex_num3 when "11";
26 |
27 | end architecture mux_logic;
28
29
```

Hex_Mux Simulation

 

Single-Bit Full Adder File

```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar|
2  library ieee;
3  use ieee.std_logic_1164.all;
4  use ieee.numeric_std.all;
5
6  library work;
7
8  entity full_adder_1bit is
9  port (
10     cin, bit_val1, bit_val2    : in std_logic;
11     bit_sum                    : out std_logic;
12     carry_out_bit              : out std_logic
13 );
14 end full_adder_1bit;
15
16 architecture Circuit of full_adder_1bit is
17     ----- Signals -----
18     -----
19     signal half_adder_sum, half_adder_carry : std_logic;
20     -----
21     -----
22     -----
23     -----
24     -----
25 begin
26     half_adder_carry    <= bit_val1 AND bit_val2;
27     half_adder_sum      <= bit_val1 XOR bit_val2;
28     bit_sum             <= half_adder_sum XOR cin;
29     carry_out_bit       <= (half_adder_sum AND cin) OR half_adder_carry;
30
31
32
33
34
35
36
37 end;
38
```


Four Bit Full Adder File

```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar
2  library ieee;
3  use ieee.std_logic_1164.all;
4  use ieee.numeric_std.all;
5
6  library work;
7
8  entity full_adder_4bit is
9  port (
10     cin          : in std_logic;
11     hex_val_A, hex_val_B : in std_logic_vector(3 downto 0);
12     hex_sum       : out std_logic_vector(3 downto 0);
13     carry_out     : out std_logic
14 );
15 end full_adder_4bit;
16
17 architecture Circuit of full_adder_4bit is
18
19     ----- Components -----
20
21
22     component full_adder_1bit
23     port (
24         cin, bit_val1, bit_val2 : in std_logic;
25         bit_sum                 : out std_logic;
26         carry_out_bit           : out std_logic
27     );
28     end component;
29
30     ----- Signals -----
31
32     ----- group of 4 logic signals with the group type defined as std_logic_vector(MSB downto LSB)
33     signal cout : std_logic_vector(3 downto 0);
34
35
36
37
```

Four Bit Full Adder File Cont.

```
38 -----
39 ----- Instances for the Full_Adder_4bit design -----
40 begin
41
42 adder0: full_adder_1bit port map (cin, hex_val_A(0), hex_val_B(0), hex_sum(0), cout(0));
43
44 adder1: full_adder_1bit port map (cout(0), hex_val_A(1), hex_val_B(1), hex_sum(1), cout(1));
45
46 adder2: full_adder_1bit port map (cout(1), hex_val_A(2), hex_val_B(2), hex_sum(2), cout(2));
47
48 adder3: full_adder_1bit port map (cout(2), hex_val_A(3), hex_val_B(3), hex_sum(3), cout(3));
49
50 carry_out <= cout(3);
51
52 end circuit;
53
```

Four-Bit Full Adder Simulation

 

Logical Processor File

```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar
2  library ieee;
3  use ieee.std_logic_1164.all;
4  library work;
5
6  entity logic_proc is
7  port (
8      logic_in0, logic_in1      : in std_logic_vector(3 downto 0);
9      logic_select              : in std_logic_vector(1 downto 0);
10     logic_out                  : out std_logic_vector(3 downto 0)
11 );
12
13 end entity logic_proc;
14
15 architecture logic_proc_logic of logic_proc is
16
17
18 begin
19
20     --for the multiplexing of two logic input busses
21     with logic_select(1 downto 0) select
22     logic_out <= (logic_in0 AND logic_in1)   when "00",
23                  (logic_in0 OR logic_in1)    when "01",
24                  (logic_in0 XOR logic_in1)   when "10",
25                  (logic_in0 XNOR logic_in1)  when "11";
26
27 end architecture logic_proc_logic;
28
29
```


Logical Processor Simulation

Logic Selector Inputs



Leds results match the outputs via the logic selector inputs for the four unique operand values

Mux_Out File

```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar|
2  library ieee;
3  use ieee.std_logic_1164.all;
4  library work;
5
6  entity mux_out is
7  port (
8      mux_num0, mux_num1          : in std_logic_vector(4 downto 0);
9      muxout_select               : in std_logic;
10     mux_out                     : out std_logic_vector(4 downto 0)
11 );
12
13 end entity mux_out;
14
15 architecture muxout_logic of mux_out is
16
17 begin
18
19     --for the multiplexing of two mux input busses
20     with muxout_select select
21     mux_out <= mux_num0 when '0',
22                mux_num1 when '1';
23
24 end architecture muxout_logic;
25
26
```

Logical Step Top

```
1  --Author: Group 3, Nandita Lohani, Puneet Bhullar|
2  library ieee;
3  use ieee.std_logic_1164.all;
4  use ieee.numeric_std.all;
5  library work;
6
7  entity LogicalStep_Lab2_top is port (
8      pb          : in  std_logic_vector(6 downto 0);    -- push buttons used for data input selection/operation control
9      sw          : in  std_logic_vector(15 downto 0);    -- The switch inputs used for data inputs
10     leds         : out std_logic_vector(5 downto 0)      -- leds for outputs
11 );
12 end LogicalStep_Lab2_top;
13
14 architecture Circuit of LogicalStep_Lab2_top is
15
16     -- Components to be Used ---
17     -----
18
19     component hex_mux
20     port (
21         hex_num3, hex_num2, hex_num1, hex_num0 : in std_logic_vector(3 downto 0);
22         mux_select                             : in std_logic_vector(1 downto 0);
23         hex_out                                : out std_logic_vector(3 downto 0)
24     );
25
26 end component;
27
28 component logic_proc
29 port (
30     logic_in0, logic_in1 : in std_logic_vector(3 downto 0);
31     logic_select         : in std_logic_vector(1 downto 0);
32     logic_out            : out std_logic_vector(3 downto 0)
33 );
34
35 end component;
36
```

Logical Step Top Cont.

```
36 |  
37 | component full_adder_4bit  
38 | port (  
39 |     cin : in std_logic;  
40 |     hex_val_A, hex_val_B : in std_logic_vector(3 downto 0);  
41 |     hex_sum : out std_logic_vector(3 downto 0);  
42 |     carry_out : out std_logic  
43 | );  
44 |  
45 | end component;  
46 |  
47 |  
48 | component mux_out  
49 | port (  
50 |     mux_num0, mux_num1 : in std_logic_vector(4 downto 0);  
51 |     muxout_select : in std_logic;  
52 |     mux_out : out std_logic_vector(4 downto 0)  
53 | );  
54 |  
55 | end component;  
56 |  
57 | ----- Signals -----  
58 |  
59 | --- groups of logic signals with each group defined as std_logic_vector(MSB downto LSB)  
60 | signal hex_A, hex_B, hex_C, hex_D : std_logic_vector(3 downto 0);  
61 |  
62 | --- some selector nets;  
63 | signal hex_mux_sel0, hex_mux_sel1, logic_proc_sel : std_logic_vector(1 downto 0);  
64 | signal hex_mux_out0, hex_mux_out1, logic_proc_out, adder_bit_out : std_logic_vector(3 downto 0);  
65 |  
66 | --- some concatenation nets  
67 | signal muxout_in0, muxout_in1 : std_logic_vector(4 downto 0);  
68 |  
69 | signal muxout_sel : std_logic;  
70 | signal carry_out : std_logic;
```


Logical Step Top Cont.

```
72
73 begin
74
75 -- assign (connect) one end of each input group (bus) to sepecific switch inputs
76 hex_A <= sw(3 downto 0);
77 hex_B <= sw(7 downto 4);
78 hex_C <= sw(11 downto 8);
79 hex_D <= sw(15 downto 12);
80
81
82 -- assign 4 of the pb inputs to drive mux selection port
83 hex_mux_sel0 <= pb(1 downto 0);
84 hex_mux_sel1 <= pb(3 downto 2);
85 logic_proc_sel <= pb(5 downto 4);
86 muxout_sel <= pb(6);
87
88 --combine singles through concatenation for the mux_out multiplexer inputs
89 muxout_in0 <= '0' & logic_proc_out;
90 muxout_in1 <= carry_out & adder_bit_out;
91
92
93 --instances for hex_mux, logic processor, full adder 4 bit and mux_out component
94 inst0: hex_mux port map (hex_A, hex_B, hex_C, hex_D, hex_mux_sel0, hex_mux_out0);
95 inst1: hex_mux port map (hex_A, hex_B, hex_C, hex_D, hex_mux_sel1, hex_mux_out1);
96
97 inst2: logic_proc port map (hex_mux_out0, hex_mux_out1, logic_proc_sel, logic_proc_out);
98 inst3: full_adder_4bit port map ('0', hex_mux_out0, hex_mux_out1, adder_bit_out, carry_out);
99
100 inst4: mux_out port map (muxout_in0, muxout_in1, muxout_sel, leds(4 downto 0));
101 leds(5) <= pb(6);
102
103
104 end Circuit;
105
106
```


Arithmetic Logic Unit Simulation

logic_select chooses any operator

mux_select chooses any operator

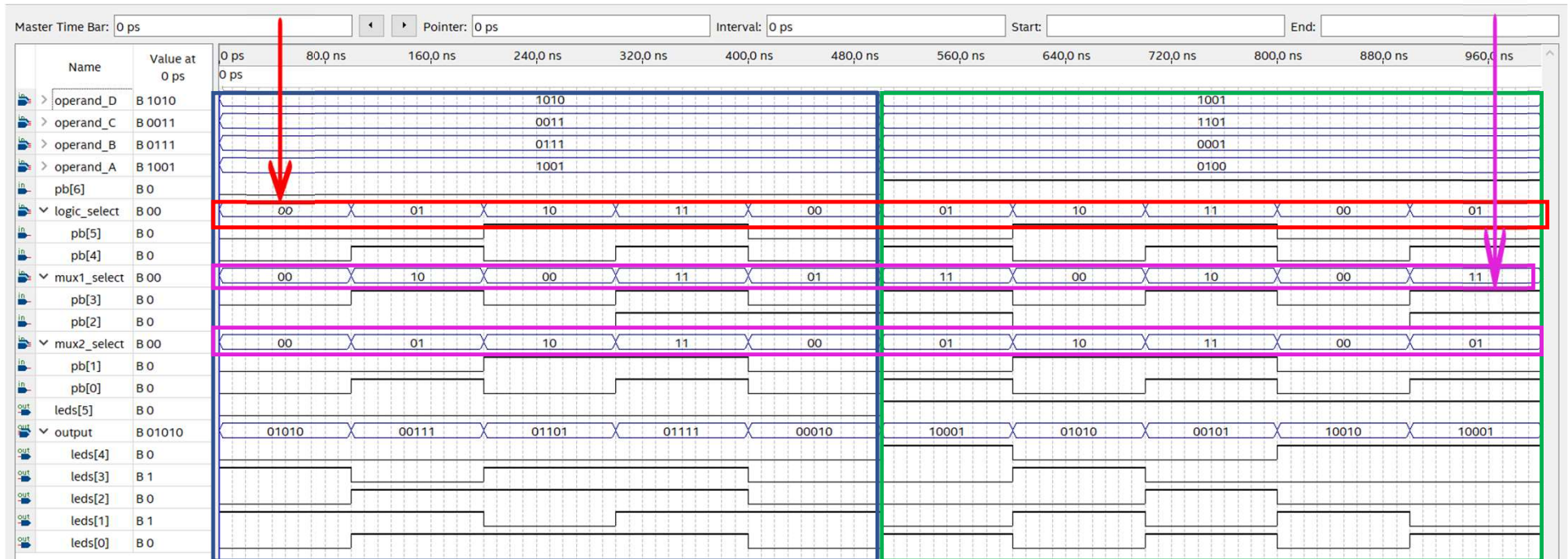

Logic Processor result is selected when pb(6) and p(5) is on

ADDER result is selected when pb(6) and p(5) is on